


Recall: Ohm's Law is stated

$$\begin{aligned} I &\propto V \\ I &= \frac{V}{R} \quad \text{rearranging} \\ I &= \left(\frac{1}{R}\right)V \end{aligned}$$

↑ constant of proportionality

Plotting current against potential difference:

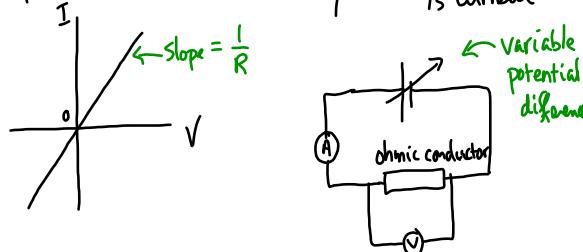
- independent variable is pot. diff / dependent variable is current



Circuit for verifying Ohm's Law.


I-V characteristics of an ohmic resistor and a filament lamp

Ohmic behaviour

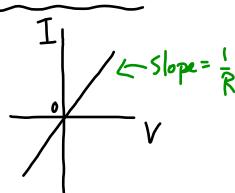

- ohmic conductor at constant temperature
- constant resistance

Non-ohmic behaviour

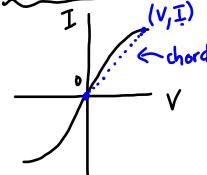

- filament lamp
- the resistance increases as the potential diff increases (or current)

* The resistance is not the reciprocal of the slope to the tangent of the curve. It is simply the value of $\frac{V}{I}$ (non-ohmic)

IF the behaviour is ohmic: Slope = $\frac{1}{R}$


$$\text{or } R = \frac{1}{\text{slope}}$$

IF the behaviour is non-ohmic, then
the slope of the chord drawn between the origin and (V, I) is $\frac{1}{R}$ or $R = \frac{1}{\text{slope (of chord)}}$


I-V characteristic of a diode

diode

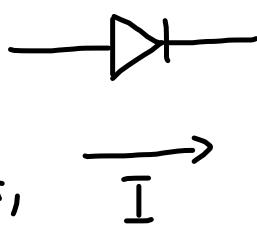A diode is a device which has a low resistance when current flows forwards through it, and a high resistance to current flowing in the opposite direction.



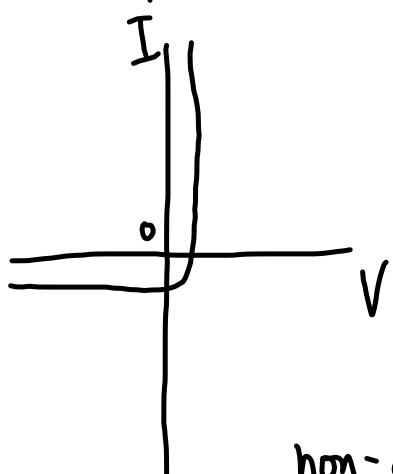\Rightarrow current essentially can only flow in one direction




non-ohmic behaviour

Why does the resistance of a metal increase as the temperature increases?

- need to look at the free electron model of conduction in a metal.

Free Electron Model of a Metal

- one or two valence electrons

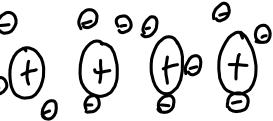

- free to move from one atom to the next along at conduction band

- think of a metal as a lattice of positive ions

in a sea of negative electrons \Rightarrow electrons are free to move around \Rightarrow delocalized electrons.

- overall, the metal is electrically neutral

- apply a potential difference to the conductor \Rightarrow electric field.

- the electric field applies a force on the electrons so they migrate in the conduction band to the positive terminal.

- the positive ions are stationary (lattice)

- the motion of the electrons under the action of the electric field is slow (they collide with the positive ions) \Rightarrow net drift of electrons toward the + terminal

- drift velocity is about 1 mm per second

- the electron drift is superimposed on the rapid thermal motion of the electrons. (much greater than the drift velocity)

- even though the drift velocity is low, the electrons all start to drift towards the positive terminal at the same time when the circuit is closed.


- when the metal's temperature increases, the random thermal motion of the electrons increases, thereby impeding the slow drift of the electrons towards the positive terminal.

\rightarrow increase the temperature of the resistor \Rightarrow increases the resistance.

Power dissipation in a resistor

For resistor, power refers to the rate at which electrical energy is converted to thermal energy.

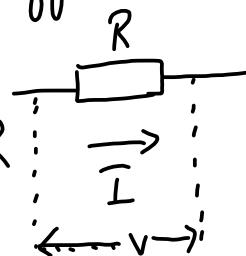When a current I flows through a resistor of resistance R due to a potential difference V , then the power dissipated is:



$$P = \frac{\Delta E_p}{\Delta t}$$

← loss in electrical potential energy of the charge Δq in time Δt

Recall: $\Delta E_p = \Delta q V$

$$P = \frac{\Delta q V}{\Delta t}$$

$$P = IV$$

Recall: $R = \frac{V}{I}$

$I = \frac{V}{R}$

$V = IR$

$$P = I(IR)$$

$$P = I^2 R$$

$$P = \left(\frac{V}{R}\right)V$$

$$P = \frac{V^2}{R}$$

Summary:

$$P = \frac{\Delta E_p}{\Delta t} = \frac{\Delta W}{\Delta t}$$

$$P = IV$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$