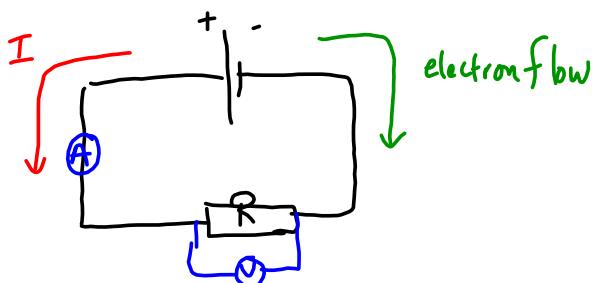



15-4 Series & Parallel Circuits

(A) Ammeter -
measures current
placed in series



(V) Voltmeter -
measures potential
difference between
2 points in the circuit
placed in parallel

Series circuit

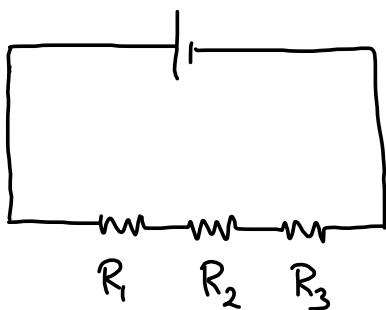

The current through each resistor is the same.

The equivalent resistance is:

$$R_{\text{TOT}} = R_1 + R_2 + R_3 + \dots + R_n$$

Adding resistors in series increases the total resistance for the circuit

MP 718


$$\left. \begin{array}{l} R_1 = 3.0\Omega \\ R_2 = 5.0\Omega \\ R_3 = 7.0\Omega \\ R_4 = 9.0\Omega \end{array} \right\} \text{series}$$

$$V = 12V$$

a) $R_{TOT} = ?$

b) $I_{TOT} = ?$

c) $V_3 = ?$

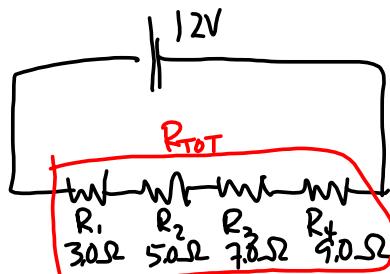

a) Series: $R_{TOT} = 3.0\Omega + 5.0\Omega + 7.0\Omega + 9.0\Omega$
 $R_{TOT} = 24.0\Omega$

b) $V = IR$

$$I = \frac{V}{R}$$

$$I = \frac{12V}{24.0\Omega}$$


$I = 0.50A$

c) $V_3 = IR_3$
 $V_3 = (0.50A)(7.0\Omega)$
 $V_3 = 3.5V$


$$\frac{1}{2}(3 + 5 + 7 + 9)$$

$$\frac{3}{2} + \frac{5}{2} + \frac{7}{2} + \frac{9}{2}$$

Parallel Circuit

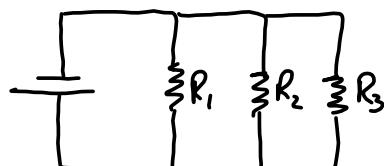

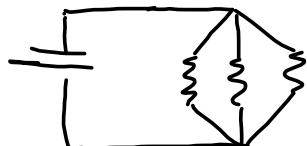In a parallel circuit, the current is divided (split) between the resistors. The potential difference across each resistor is the same.




$$\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

Adding resistors in parallel reduces the overall resistance.

MP|722

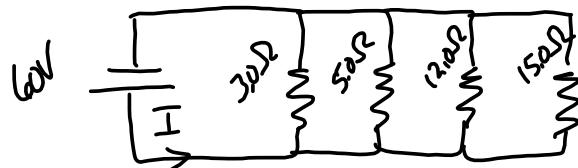3.0Ω, 5.0Ω, 12.0Ω, 15.0Ω
parallel
 $V = 60V$



a) $R_{TOT} = ?$

b) $I_{TOT} = ?$

c) $I_{12.0} = ?$

a) $R_{TOT} \Rightarrow$

$$\frac{1}{R_{TOT}} = \frac{1}{3.0\Omega} + \frac{1}{5.0\Omega} + \frac{1}{12.0\Omega} + \frac{1}{15.0\Omega}$$

$$\frac{1}{R_{TOT}} = 0.68\Omega^{-1}$$

$$R_{TOT} = 1.46\Omega$$

b) $V = IR$

$$I = \frac{V}{R}$$

$$I = \frac{60V}{1.46\Omega}$$

$$I = 41A$$


c) $V = IR$

$$I = \frac{V}{R}$$

$$I = \frac{60V}{12.0\Omega}$$

$$I = 5.0A$$

for 12.0Ω

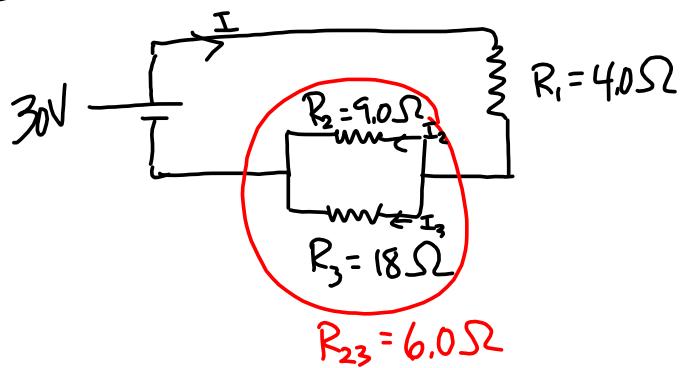Complex Circuit

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{23}} = \frac{1}{9.0\Omega} + \frac{1}{18\Omega}$$

$$\frac{1}{R_{23}} = 0.17\Omega^{-1}$$

$$R_{23} = 6\Omega$$

$$R_{TOT} = R_1 + R_{23}$$

$$R_{TOT} = 4.0\Omega + 6.0\Omega$$

$$R_{TOT} = 10.0\Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_{TOT} = \frac{30V}{10.0\Omega}$$

$$I_{TOT} = 3.0A$$

Resistor 1

$$I_1 = 3.0A$$

$$R_1 = 4.0\Omega$$

$$V = ?$$

$$V = IR$$

$$V = (3.0A)(4.0\Omega)$$

$$V = 12V$$

Resistor 2

$$V = 18V$$

$$I = ?$$

$$R = 9.0\Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{18V}{9.0\Omega}$$

$$I = 2.0A$$

Resistor 3

$$V = 18V$$

$$I = ?$$

$$R = 18\Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{18V}{18\Omega}$$

$$I_3 = 1.0A$$