


## Internal Resistance

Recall the circuit equation:

$$\mathcal{E} = \textcircled{V} + Ir$$

$IR$

$$\mathcal{E} = V + Ir$$

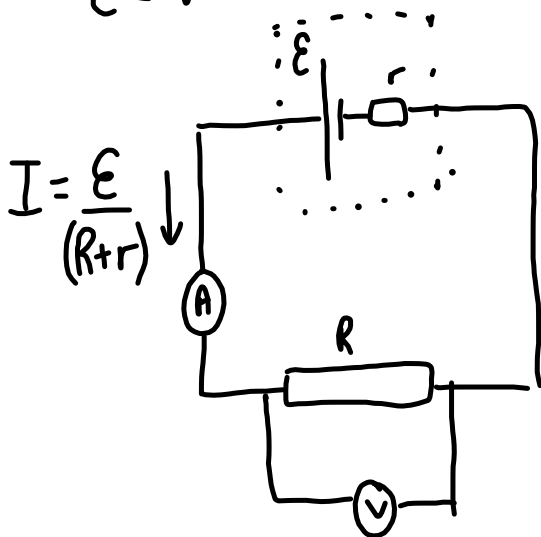

$$I = \frac{\mathcal{E}}{R+r}$$

$$\mathcal{E} = IR + Ir$$

$$\mathcal{E} = I(R+r)$$

Dosta Booklets


$$V = \mathcal{E} - Ir$$

Example

In the circuit shown, the cell has an emf of 1.8V and an internal resistance of  $0.60\Omega$

$$\underline{I} = \frac{V}{R}$$

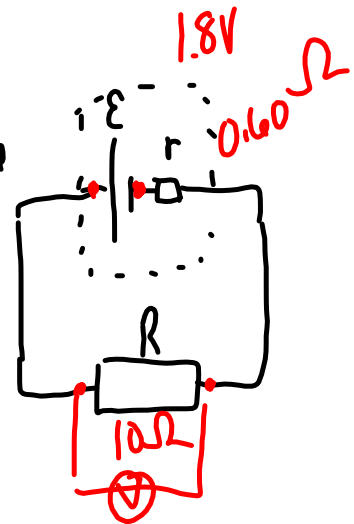Find the potential difference across the cell terminals and the current drawn if the value of  $R$  is  $10\Omega$



$$\mathcal{E} = I(R+r)$$

$$I = \frac{\mathcal{E}}{R+r}$$

$$I = \frac{1.8V}{(10\Omega + 0.60\Omega)}$$

$$I = 0.17A$$

$$V = \mathcal{E} - Ir$$

$$V = 1.8V - (0.17A)(0.60\Omega)$$

$$V = 1.7V$$

Example

A photoelectric cell can draw a current of  $0.10\text{ A}$  when driving a small load of resistance  $2.0\ \Omega$ . If the emf of the cell is shown  $0.8\text{ V}$ , determine its internal resistance under these conditions.

$$I = 0.10\text{ A}$$

$$R = 2.0\ \Omega$$

$$\mathcal{E} = 0.8\text{ V}$$

$$r = ?$$

$$\mathcal{E} = I(R + r)$$

$$\frac{\mathcal{E}}{I} = R + r$$

$$r = \frac{\mathcal{E}}{I} - R$$

$$r = \frac{0.8\text{ V}}{0.10\text{ A}} - 2.0\ \Omega$$

$$r = 8.0\ \Omega - 2.0\ \Omega$$

$$r = 6.0\ \Omega$$

Example

A cell has an internal resistance of  $0.45\ \Omega$ . The potential difference across its terminals is  $1.35\text{ V}$  when a current of  $0.18\text{ A}$  is being drawn from it.

What is the EMF of the cell?

$$r = 0.45\ \Omega$$

$$V = 1.35\text{ V}$$

$$I = 0.18\text{ A}$$

$$\mathcal{E} = ?$$

$$\mathcal{E} = V + Ir$$

$$\mathcal{E} = 1.35\text{ V} + (0.18\text{ A})(0.45\ \Omega)$$

$$\mathcal{E} = 1.4\text{ V}$$

When a battery goes dead .....


- its emf doesn't change but its internal resistance increases.
- if we measure the internal resistance of a cell or a battery, we can see if it is dead or not

### Measurement of internal resistance

- We need to measure current and potential difference:

- When the switch  $S$  is open no current flows so there is no energy lost in the internal

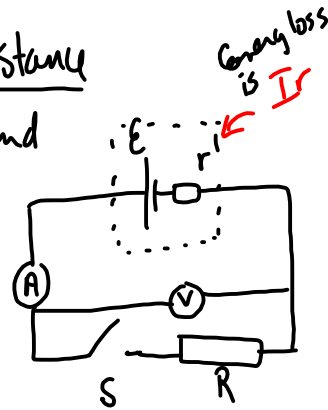resistance ( $Ir = 0$ ) and the voltmeter reads the emf of the cell.



$$V = \mathcal{E} - Ir \leftarrow 0$$

$$V = \mathcal{E} \leftarrow \text{only if no current (switch is open)}$$

- If the switch is closed, the current  $I$  flows and now the potential difference will be less than the emf.

$$V = \mathcal{E} - Ir$$

$$Ir = \mathcal{E} - V$$

$$r = \frac{\mathcal{E} - V}{I}$$

If  $r$  is large, then  $V \ll \mathcal{E}$

If  $r$  is zero, then  $V = \mathcal{E}$

Example

A voltmeter connected across the terminals of a battery reads  $7.5\text{V}$ . When the battery is connected to a load, the voltage reading across the terminal is  $6.2\text{V}$  and the current flowing is  $0.65\text{A}$ . Calculate the internal resistance of the battery under these conditions.

$$\mathcal{E} = 7.5\text{V}$$

$$V = 6.2\text{V}$$

$$I = 0.65\text{A}$$

$$r = ?$$


$$r = \frac{\mathcal{E} - V}{I}$$

$$r = \frac{7.5\text{V} - 6.2\text{V}}{0.65\text{A}}$$

$$r = 2.0\Omega$$

Measurement of internal resistance - graphical method

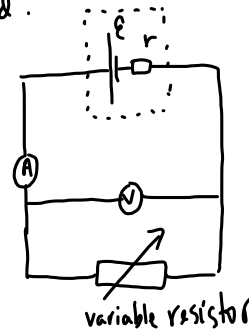- measure the potential difference across the terminals of a battery as the current is changed.
- the current is varied by changing the resistance. (independent variable)
- the potential difference is the dependent variable.



$$V = \mathcal{E} - Ir$$


$$(y = b + mx)$$

$$\textcircled{V} = -r\textcircled{I} + \mathcal{E}$$

$$(y = mx + b)$$

V vs I  
is linear

slope is -r  
y-int is  $\mathcal{E}$

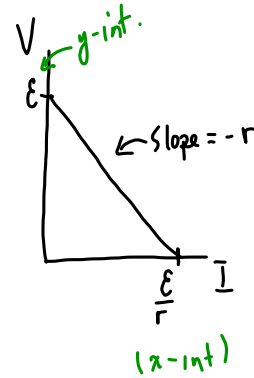


Recall from Ohm's Law: I vs V was linear

(here we changed V and measured I)

Now for internal resistance: V vs I (we are changing the current and measuring V)

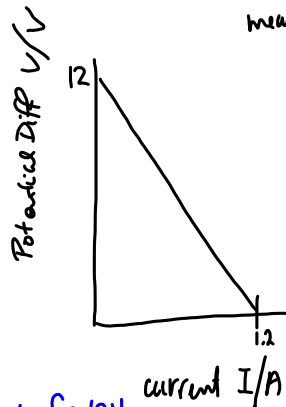Example

Determine the emf and the internal resistance of the battery



Emf is the y-intercept  $\therefore \mathcal{E} = 12V$

slope = -r

$$\begin{aligned} \text{slope} &= \frac{-12V}{1.2A} \\ &= -10\Omega \end{aligned}$$


$$\therefore -r = -10\Omega$$

$$\boxed{r = 10\Omega}$$

## Power

- Power delivered by the battery:

$$P = \epsilon I$$

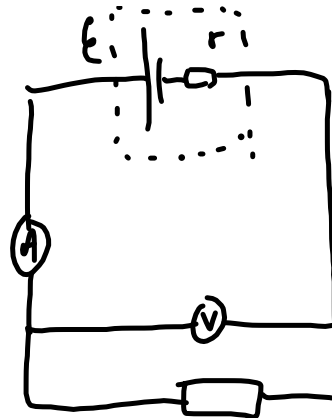

- Power generated in the resistor is

$$P = VI$$

- Power lost as heat generated in the battery

$$P = I^2 r$$

$$\text{Power battery} = \text{Power in } R + \text{Power in } r$$

$$\cancel{\epsilon I} = \cancel{VI} + \cancel{I^2} r$$

$$\epsilon = V + Ir$$

↳ The circuit equation.